



Princess Sumaya  
University  
for Technology

## King Abdullah II School of Engineering

EE21221

Electric Circuits (1)

Section #34

Quiz # 2

Wednesday 17/11/2021

Name: .....

Q.1) Find  $i_8$ ,  $i_4$ ,  $i_{10}$ ,  $i_2$ ,  $v_8$ ,  $v_4$ ,  $v_{10}$ , and  $P_{ix}$  in the circuit shown in Figure Q.1. [8-Points]

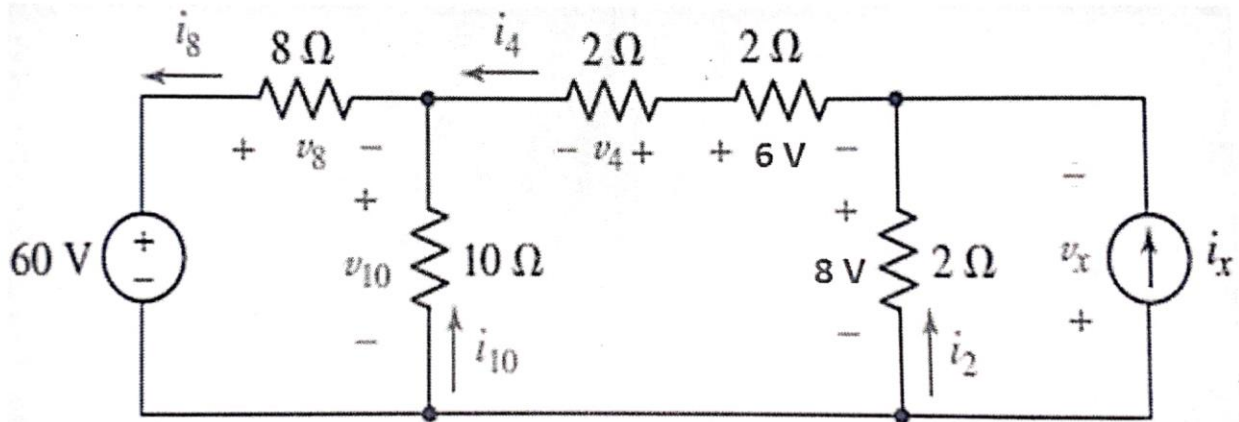


Figure Q.1

Solution:

$$i_8 = -5A$$

$$i_4 = -3A$$

$$i_{10} = -2A$$

$$i_2 = -4A$$


$$v_8 = 40V$$

$$v_4 = -6V$$


$$v_{10} = 20V$$

$$P_{ix} = -8W$$

Q1)

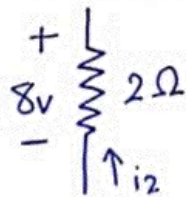


$$i_2 = \frac{-8}{2} = -4A$$

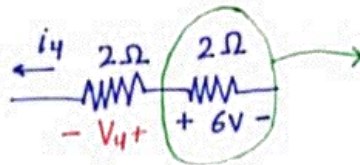

$$i_4 = \frac{-6}{2} = -3A$$

→ Same current & same resistance  $|V_4| = 6V$

$$V_4 = -6V$$

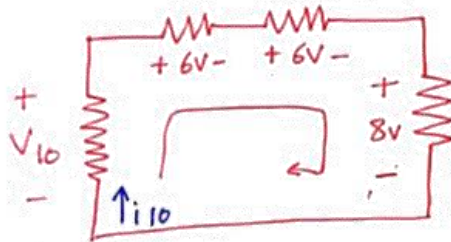


KVL

$$-V_{10} + 6 + 6 + 8 = 0$$

$$V_{10} = 20V$$

$$i_{10} = \frac{-20}{10} = -2A$$

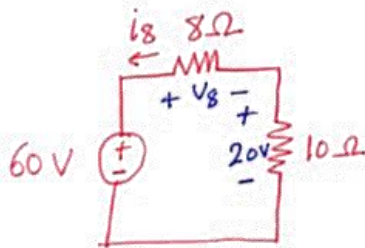

$$-60 + V_8 + 20 = 0$$


$$V_8 = 40V$$

$$i_8 = \frac{-40}{8} = -5A$$

$$i_x + (-4) - (-3) = 0$$

$$i_x - 1 = 0$$

$$i_x = 1$$

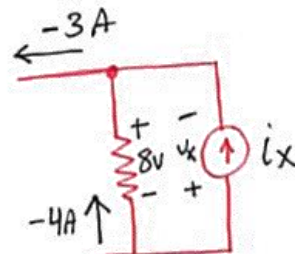

$$V_x = -8V$$

$$P_{ix} = (-8)(1) = -8W$$

↓  
supply

Q.2) In the circuit shown in Figure Q.2, find  $v_{R2}$ . [2-Points]

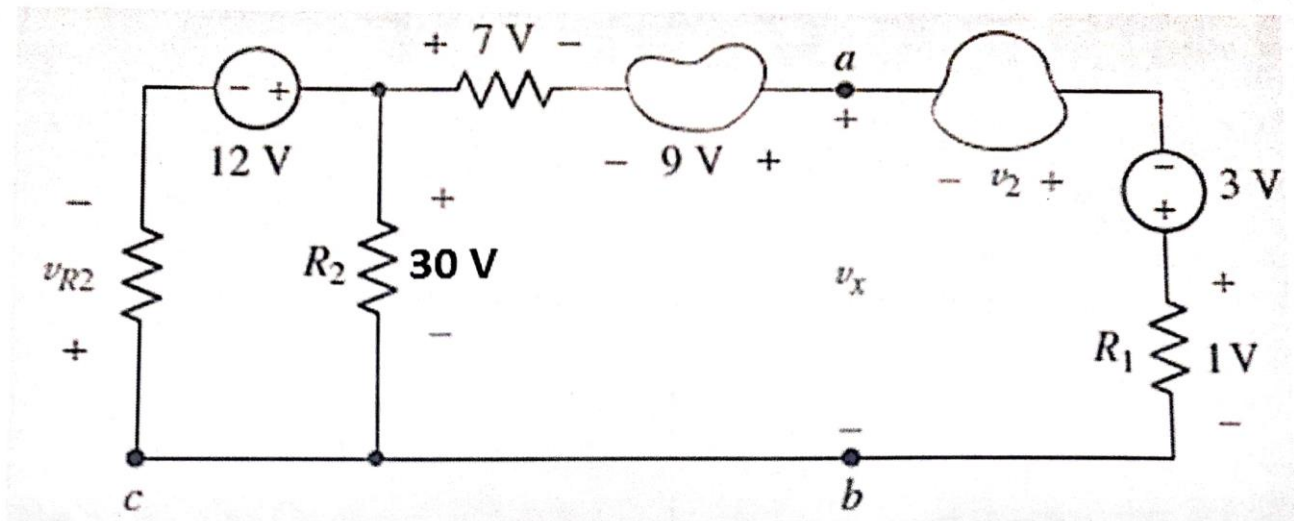


Figure Q.2

Solution:

$v_{R2} =$

$-18V$

KVL

$$+v_{R2} - 12 + 30 = 0$$

$$v_{R2} = -18V$$